

P01 report

Muhammed Juneer

march 2019

Chapter 1

Theoretical part

1.1 Circuit calculation

Theoretical calculation of the circuit $V1=1.7V$ $R1 = 2\Omega$ $R2=8\text{ohm}$

$$VR = (R \times VT)/RT$$

$$VR1 = (R1 \times V1)/RT = V$$

$$VR2 = (R2 \times V2)/RT = V$$


 


Figure 1.1: Electrical circuit diagram

V1	V
R1	ohm
R2	ohm
UR1	V
UR2	V

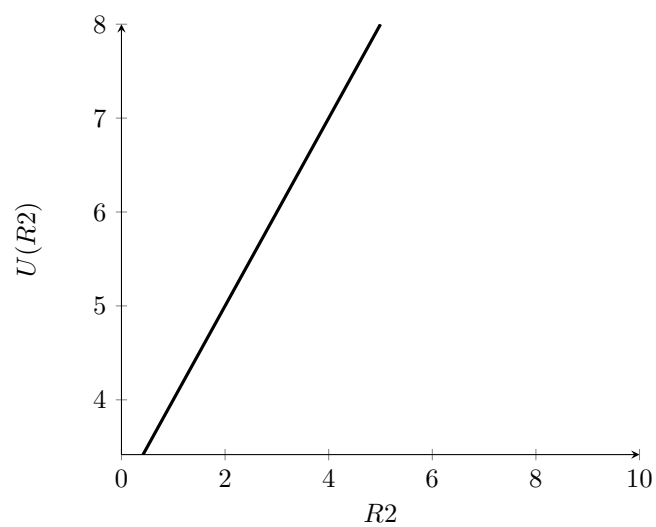

Chapter 2


Practical part

Practical Calculation

2.1 Work with GEDA programs'


2.1.1 'Work with gschem'

Figure 2.1: Circuit Diagram createed in gscehm

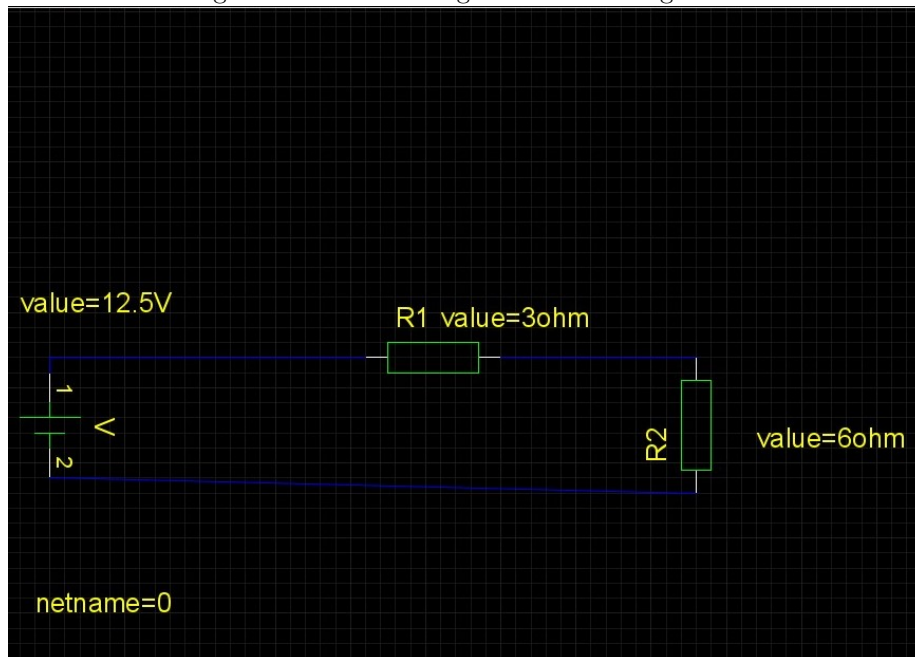

2.1.2 'Work with gnetlist'

Figure 2.2: The plotted graph after using ngspice

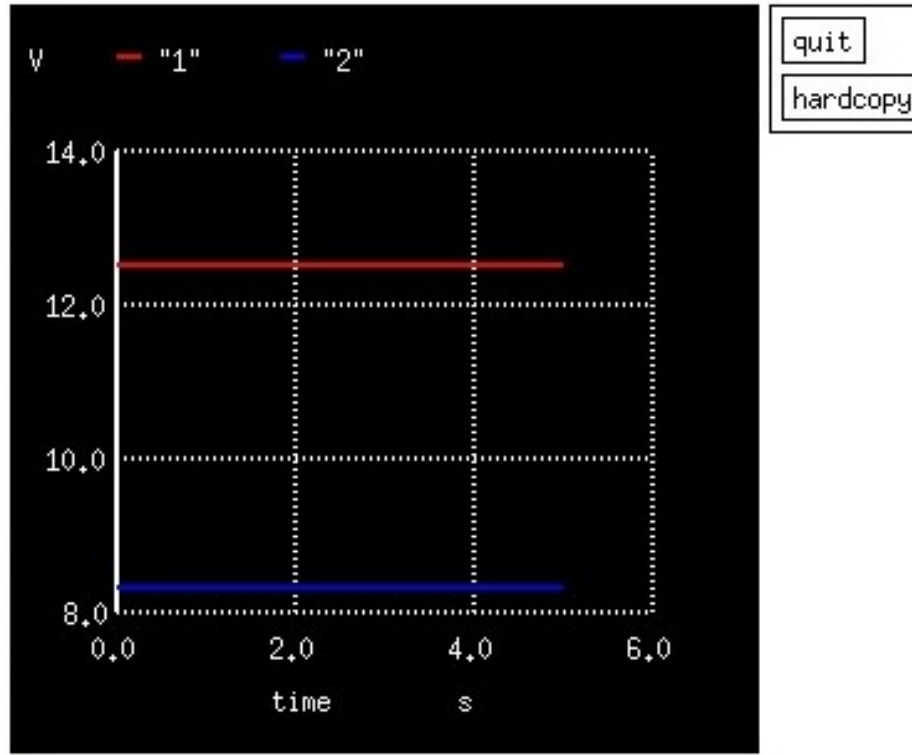

2.2 'Work with QUCS programs'

Image of Schematics

DC simulation

Curve and Table obtained from DC Simulation

Figure 2.3: Circuit Diagram in QUCS

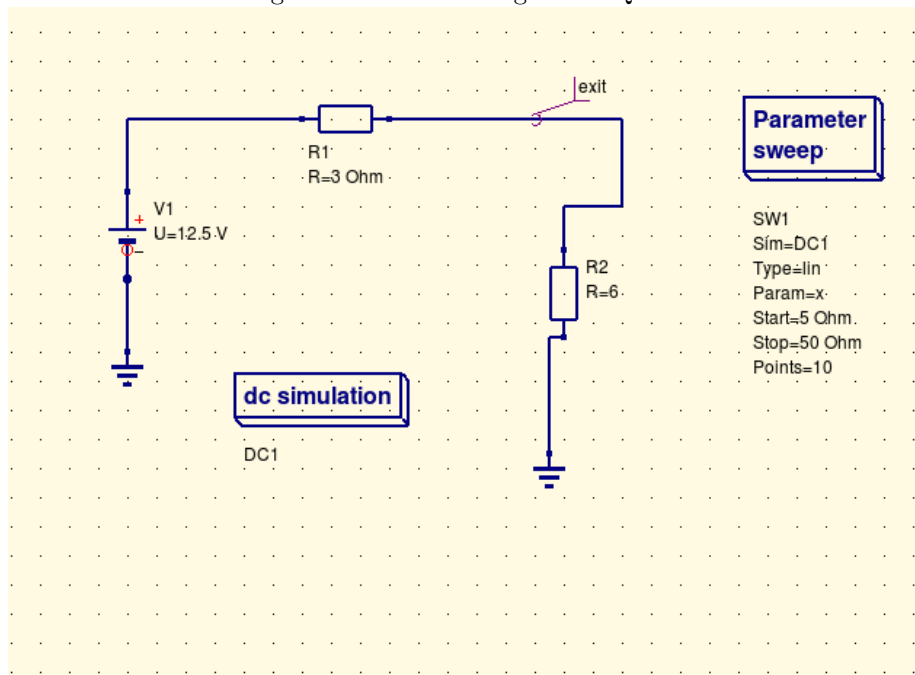


Figure 2.4: DC Simulation



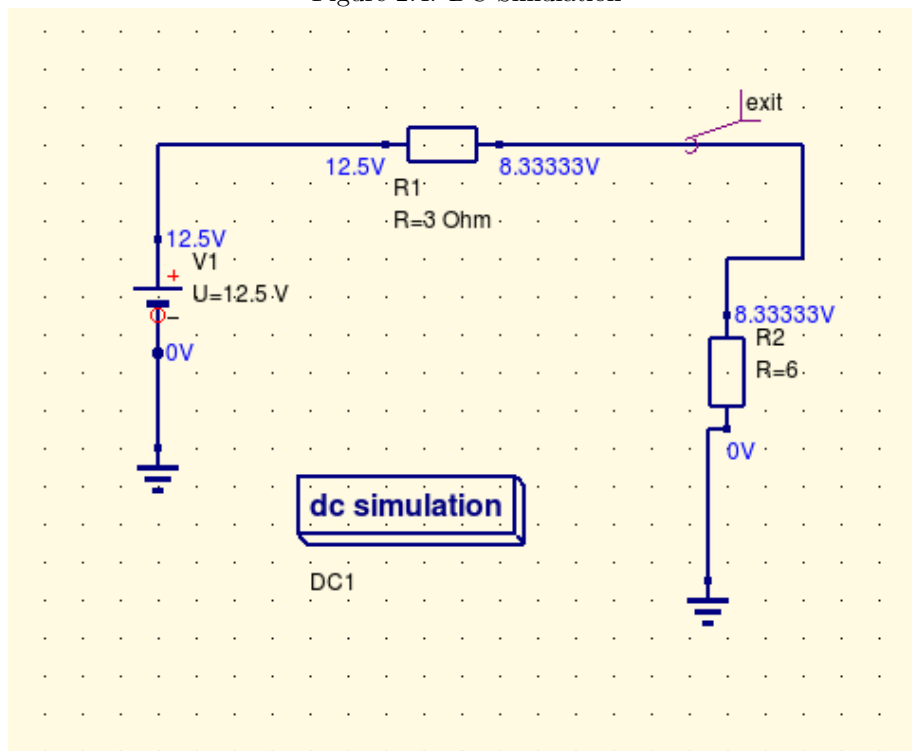


Figure 2.5: The following graph shows the DC simulation for the various obtained values

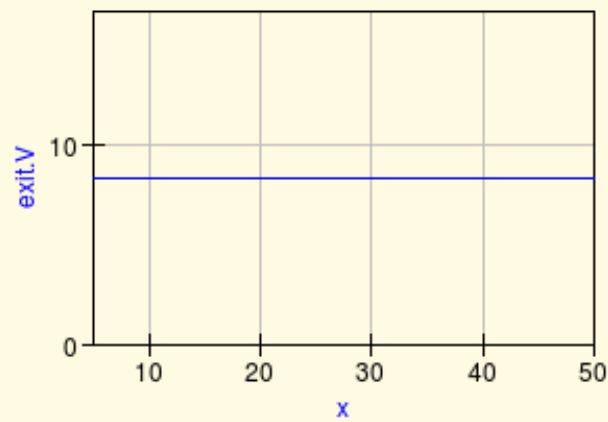

x	V1.I	x
5	-1.39	→
10	-1.39	
15	-1.39	
20	-1.39	
25	-1.39	
30	-1.39	
35	-1.39	
40	-1.39	
45	-1.39	
50	-1.39	

Figure 2.6: The following graph shows the Sweep Simulation for the various obtained values

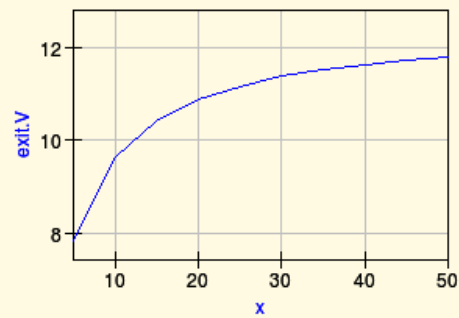

Equation
UR2=f(R2)

x	V1.I	
5	-1.56	
10	-0.962	
15	-0.694	
20	-0.543	
25	-0.446	
30	-0.379	
35	-0.329	
40	-0.291	
45	-0.26	
50	-0.236	